

# 22320

11819

**3 Hours / 70 Marks**

Seat No.

--	--	--	--	--	--	--	--

- Instructions* –
- (1) All Questions are *Compulsory*.
  - (2) Answer each next main Question on a new page.
  - (3) Illustrate your answers with neat sketches wherever necessary.
  - (4) Figures to the right indicate full marks.
  - (5) Assume suitable data, if necessary.
  - (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

**Marks**

- 1. Attempt any FIVE of the following:** **10**
- a) Write the radix of binary, octal, decimal and hexadecimal number system.
  - b) Draw the circuit diagram for AND and OR gates using diodes.
  - c) Write simple examples of boolean expression for SOP and POS.
  - d) State the necessity of multiplexer.
  - e) Draw logic diagram of T flip-flop and give its truth table.
  - f) Define modulus of a counter. Write the numbers of flip flops required for Mod-6 counter.
  - g) State function of preset and clear in flip flop.

P.T.O.

2. **Attempt any THREE of the following:** 12
- Draw the block diagram of Programmable Logic Array.
  - Convert -
    - $(255)_{10} = ( ? )_{16} = ( ? )_8$
    - $(157)_{10} = ( ? )_{\text{BCD}} = ( ? )_{\text{Excess3}}$
  - Draw the symbol, truth table and logic expression of any one universal logic gate. Write reason why it is called universal gate.
  - Minimize the following expression using K-Map.  
 $f(A, B, C, D) = \Sigma m (0, 1, 2, 4, 5, 7, 8, 9, 10)$
3. **Attempt any THREE of the following:** 12
- Compare TTL and CMOS logic families on the basis of following:
    - Propagation delay
    - Power Dissipation
    - Fan-out
    - Basic gate
  - Describe the function of Full Adder Circuit using its truth table, K-Map simplification and logic diagram.
  - Realize the basic logic gates, NOT, OR and AND gates using NOR gates only.
  - Describe the working of JK flip-flop with its truth table and logic diagram.
4. **Attempt any THREE of the following:** 12
- Draw and explain working of 4 bit serial Input parallel Output shift register.
  - Draw 16:1 MUX tree using 4:1 MUX.
  - Calculate analog output of 4 bit DAC for digital input 1101. Assume  $V_{\text{FS}} = 5\text{V}$ .
  - State De Morgan's theorem and prove any one.
  - Design one digit BCD Adder using IC 7483.

**5. Attempt any TWO of the following:****12**

- a) Subtract using 2's compliment method  
 $(35)_{10} - (5)_{10}$
- b) Design a 4 bit synchronous counter and draw its logic diagram.
- c) Describe the working of successive Approximation ADC. Define Resolution and conversion time associated with ADC.

**6. Attempt any TWO of the following:****12**

- a) Design 4 bit Binary to Gray code converter.
  - b) Compare the following (Any three points)
    - (i) Volatile with Non-volatile memory
    - (ii) SRAM with DRAM memory
  - c) Give block schematic of decade counter IC 7490. Design Mod-7 counter using this IC.
-